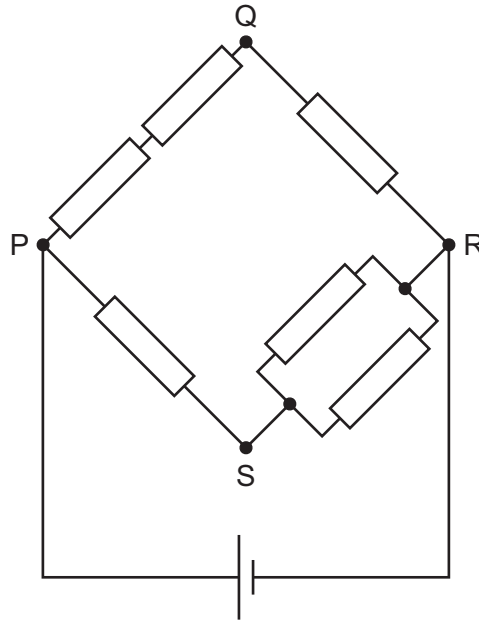


**34** The diagram shows six identical resistors connected in a circuit.



In which branch of the circuit is the most power dissipated?

**A** PQ

**B** QR

**C** RS

**D** SP