

- 6 (a) Define *charge*.

..... [1]

- (b) A heater is made from a wire of resistance $18.0\ \Omega$ and is connected to a power supply of 240 V. The heater is switched on for 2.60 Ms.

Calculate

- (i) the power transformed in the heater,

power = W [2]

- (ii) the current in the heater,

current = A [1]

- (iii) the charge passing through the heater in this time,

charge = C [2]

- (iv) the number of electrons per second passing a given point in the heater.

number = s^{-1} [2]

For
Examiner's
Use