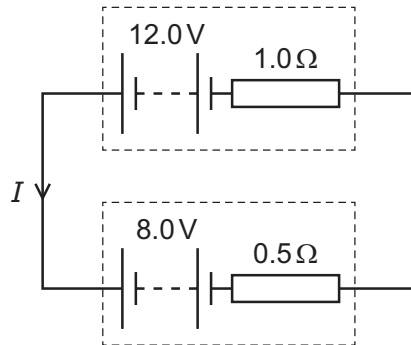


35 The diagram shows a circuit containing two batteries connected together.



What is the current I ?

- A** 2.7 A **B** 4.0 A **C** 8.0 A **D** 13 A