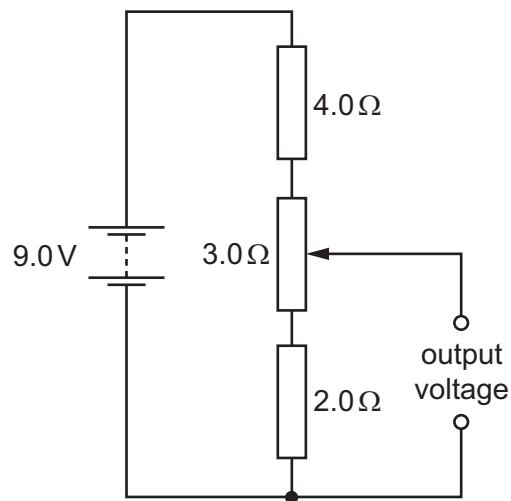


- 36** A potential divider circuit consists of fixed resistors of resistance  $2.0\ \Omega$  and  $4.0\ \Omega$  connected in series with a  $3.0\ \Omega$  resistor fitted with a sliding contact. These are connected across a battery of e.m.f.  $9.0\ \text{V}$  and zero internal resistance, as shown.



What are the maximum and the minimum output voltages of this potential divider circuit?

	maximum voltage / V	minimum voltage / V
<b>A</b>	4.0	2.0
<b>B</b>	5.0	2.0
<b>C</b>	9.0	0
<b>D</b>	9.0	2.0

- 37** A cell of e.m.f.  $2.0\ \text{V}$  and negligible internal resistance is connected to a network of resistors as