

36 What is the circuit symbol for an oscilloscope?

A



B



C



D



37 The circuit below has a battery of e.m.f. 6.0 V and a variable resistor. The variable resistor is set to 10 Ω. The circuit is connected to a voltmeter. The voltmeter reads 2.0 V. What is the resistance of the variable resistor?