

- 6 (a) Define *electric potential difference* (p.d.).

.....
..... [1]

- (b) A wire of cross-sectional area A is made from metal of resistivity ρ . The wire is extended. Assume that the volume V of the wire remains constant as it extends.

Show that the resistance R of the extending wire is inversely proportional to A^2 .

[2]

- (c) A battery of electromotive force (e.m.f.) E and internal resistance r is connected to a variable resistor of resistance R , as shown in Fig. 6.1.

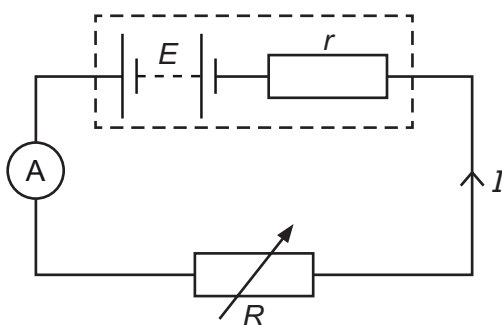


Fig. 6.1

The current in the circuit is I .

Use Kirchhoff's second law to show that

$$R = \left(\frac{E}{I} \right) - r.$$

[1]

- (d) An ammeter is used in the circuit in (c) to measure the current I as resistance R is varied. Fig. 6.2 is a graph of R against $\frac{1}{I}$.

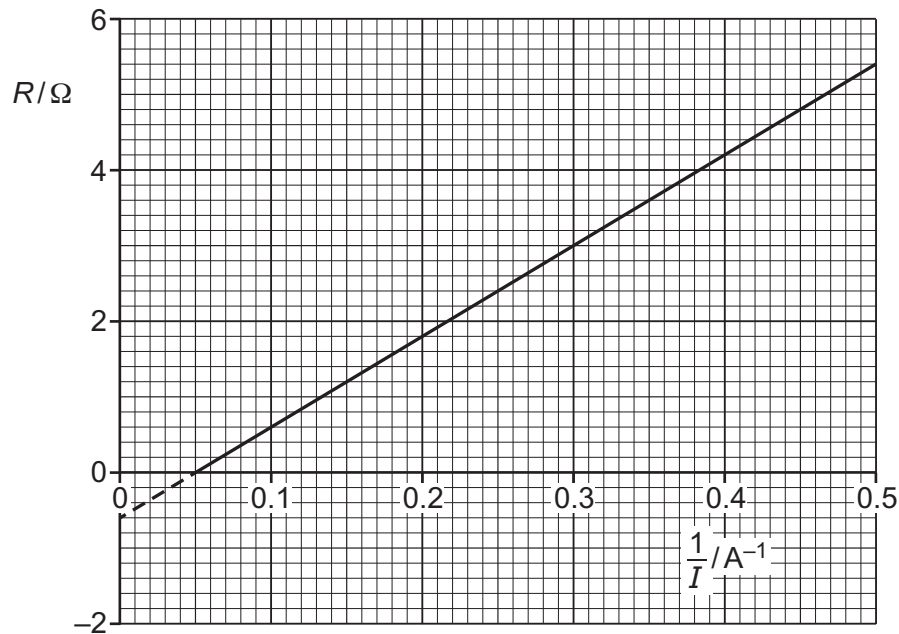


Fig. 6.2

- (i) Use Fig. 6.2 to determine the power dissipated in the variable resistor when there is a current of 2.0 A in the circuit.

power = W [3]

- (ii) Use Fig. 6.2 and the equation in (c) to:

1. state the internal resistance r of the battery

$r = \dots \Omega$

2. determine the e.m.f. E of the battery.

$E = \dots \text{ V}$
[3]