

**37** In the circuits shown, the cell has negligible internal resistance.

Which diagram shows a potential divider circuit that can vary the potential difference (p.d.) across the lamp?

