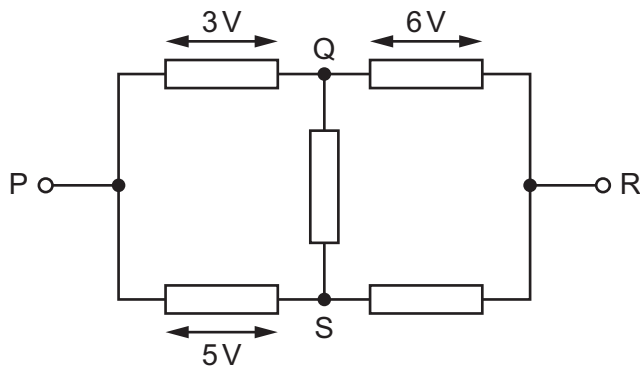


**35** There is a current from P to R in the resistor network shown.



The potential difference (p.d.) between P and Q is 3 V.

The p.d. between Q and R is 6 V.

The p.d. between P and S is 5 V.

Which row in the table is correct?

	p.d. between Q and S	p.d. between S and R
<b>A</b>	2 V	4 V
<b>B</b>	2 V	10 V
<b>C</b>	3 V	4 V
<b>D</b>	3 V	10 V