

8 Fig. 8.1 shows a circuit that produces rectification of an alternating input voltage.

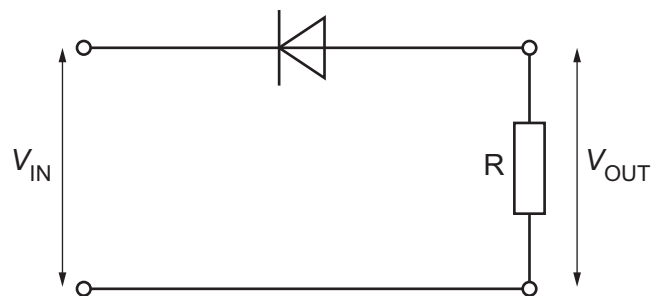


Fig. 8.1

The input voltage  $V_{IN}$  is sinusoidal. The rectified output voltage  $V_{OUT}$  is applied across resistor  $R$ .

The variation of  $V_{IN}$  with time  $t$  has amplitude  $V_0$  and period  $T$ , as shown in Fig. 8.2.

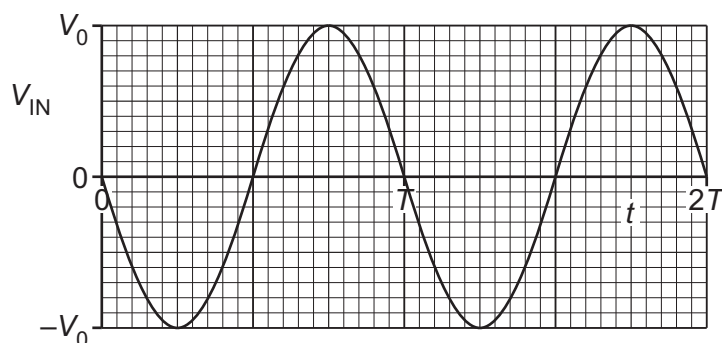


Fig. 8.2

The root-mean-square (r.m.s.) value of  $V_{IN}$  is  $6.0\text{ V}$ .

(a) (i) State the type of rectification produced by the circuit of Fig. 8.1.

..... [1]

(ii) Calculate  $V_0$ .

$V_0 = \dots\dots\dots \text{ V [1]}$



(b) Resistor R has resistance  $45\ \Omega$ .

Assume that there is no p.d. across the diode when it is conducting.

(i) Determine the peak power  $P_0$  in the resistor.

$P_0 = \dots\dots\dots$  W [2]

(ii) On Fig. 8.3, sketch the variation of the power  $P$  in the resistor with  $t$  between  $t = 0$  and  $t = 2T$ .

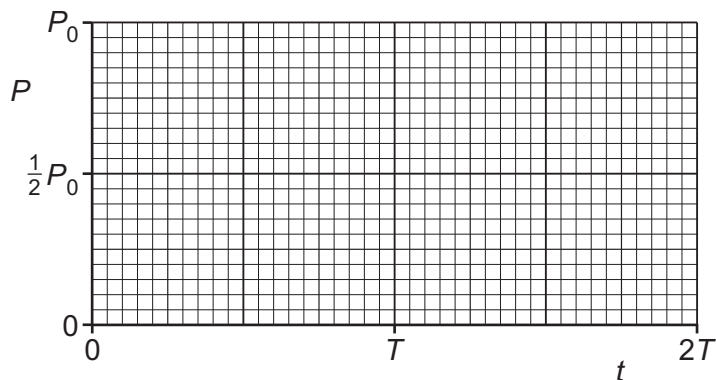


Fig. 8.3

[3]

(iii) Use the answer in (b)(ii) to explain why the mean power in the resistor is  $\frac{1}{4}P_0$ .

.....  
 .....  
 ..... [2]

(iv) Use the information in (b)(iii) to determine the r.m.s. value of  $V_{OUT}$ .

r.m.s. voltage = ..... V [1]