

- 6 (a) State Faraday's law of electromagnetic induction.

For
Examiner's
Use

.....

 [2]

- (b) The output of an ideal transformer is connected to a bridge rectifier, as shown in Fig. 6.1.

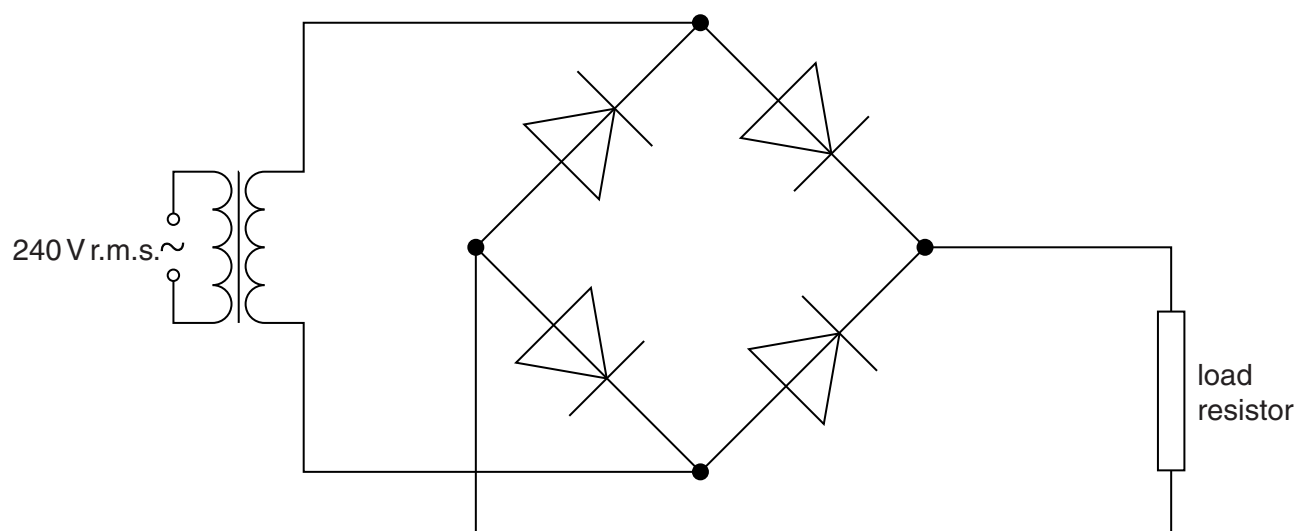


Fig. 6.1

The input to the transformer is 240 V r.m.s. and the **maximum** potential difference across the load resistor is 9.0 V.

- (i) On Fig. 6.1, mark with the letter P the positive output from the rectifier. [1]
 (ii) Calculate the ratio

$$\frac{\text{number of turns on primary coil}}{\text{number of turns on secondary coil}}$$

ratio = [3]

- (c) The variation with time t of the potential difference V across the load resistor in (b) is shown in Fig. 6.2.

For
Examiner's
Use

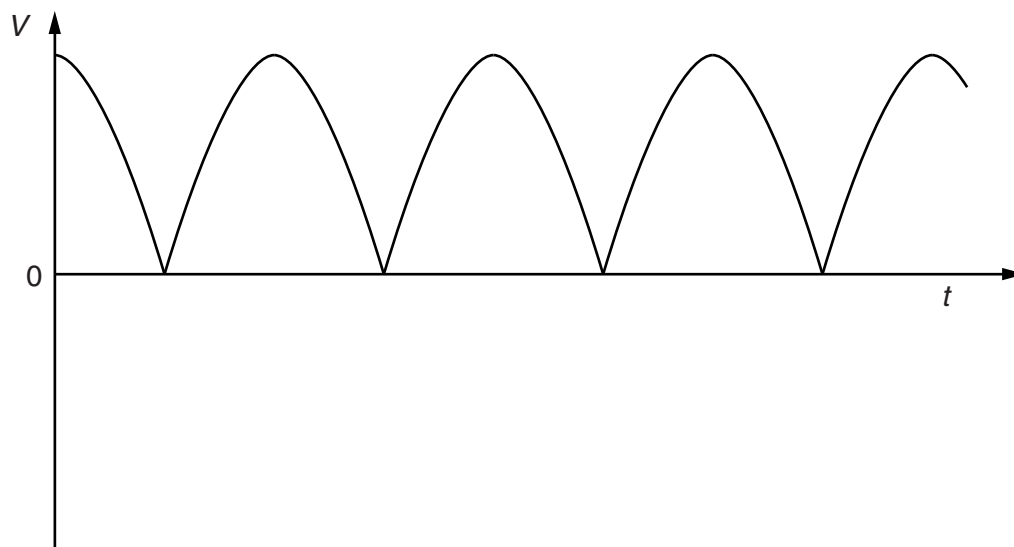


Fig. 6.2

A capacitor is now connected in parallel with the load resistor to produce some smoothing.

- (i) Explain what is meant by *smoothing*.

.....
 [1]

- (ii) On Fig. 6.2, draw the variation with time t of the smoothed output potential difference. [2]