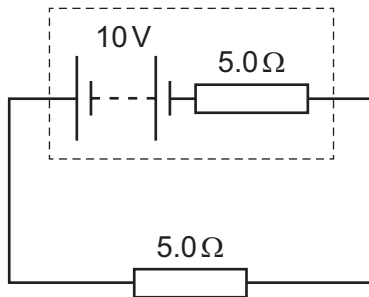


- 34** A battery of electromotive force (e.m.f.) 10 V and internal resistance $5.0\ \Omega$ is connected to a $5.0\ \Omega$ load resistor.



Which change occurs when the $5.0\ \Omega$ load resistor is replaced with a $50\ \Omega$ load resistor?

- A** The current in the circuit increases.
- B** The potential difference across the load resistor increases.
- C** The power dissipated in the internal resistance of the battery increases.
- D** The total power dissipated in the circuit increases.