

32 Which graph represents the way the current I through a filament lamp varies with the potential difference V across it?

