

**33** The diagrams show connected wires which carry currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ .

The currents are related by the equation  $I_1 + I_2 = I_3 + I_4$ .

To which diagram does this equation apply?

