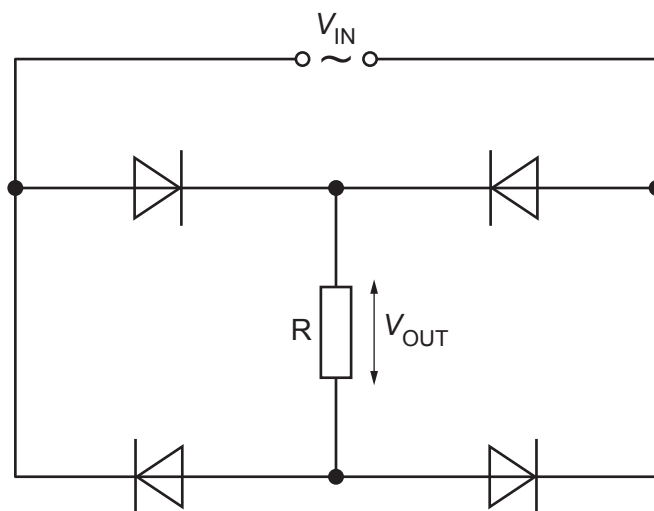


- 7 A circuit contains a power supply that provides a sinusoidal alternating input voltage  $V_{IN}$ . There is an output voltage  $V_{OUT}$  across a load resistor  $R$ , as shown in Fig. 7.1.



**Fig. 7.1**


- (a) State the purpose of the circuit in Fig. 7.1.

.....

.....

..... [2]

- (b) Fig. 7.2 shows the variation of  $V_{OUT}$  with time  $t$ .

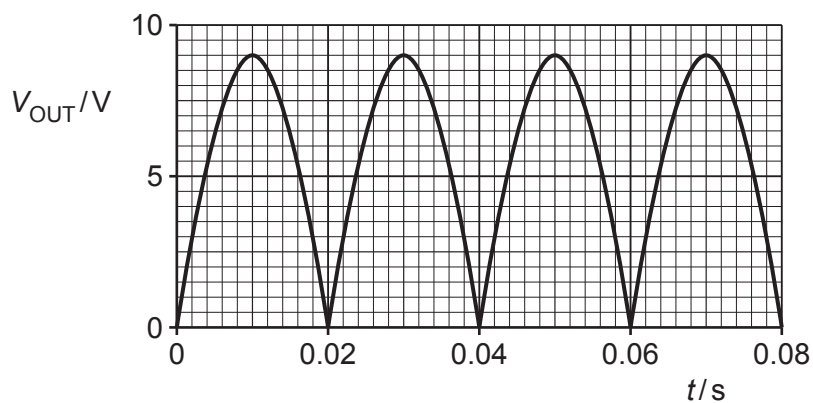


**Fig. 7.2**

- (i) The load resistor  $R$  has a resistance of  $370\ \Omega$ .

Show that the maximum power dissipated in  $R$  is  $0.22\text{ W}$ .

[2]

- (ii) On Fig. 7.3, sketch the variation with  $t$  of the power  $P$  dissipated in  $R$ .

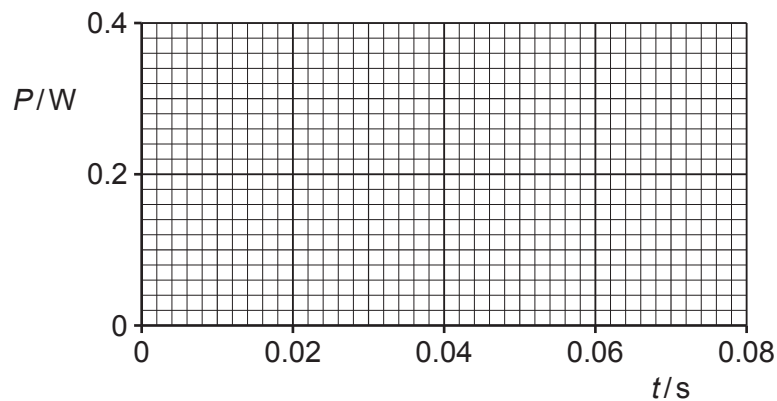

**Fig. 7.3**

[3]

- (iii) Calculate the mean power dissipated in  $R$ .

mean power = ..... W [1]

- (c) The circuit of Fig. 7.1 is disconnected, and  $R$  is connected directly across the power supply.

Explain, without calculation, how the mean power now dissipated in  $R$  compares with the answer in **(b)(iii)**.

.....

.....

..... [2]