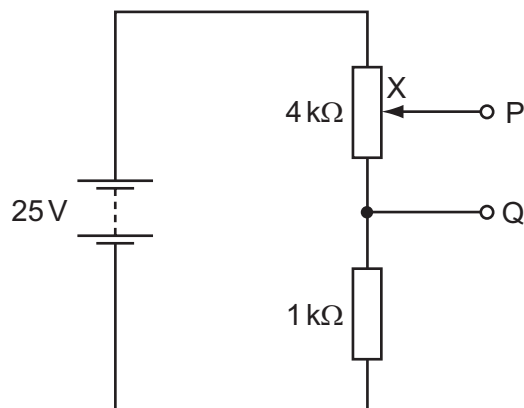


- 37** The diagram shows a potential divider circuit which, by adjustment of the contact X, can be used to provide a variable potential difference between the terminals P and Q.



What are the limits of this potential difference?

- A** 0 and 5 V **B** 0 and 20 V **C** 0 and 25 V **D** 5 V and 25 V

Space for working