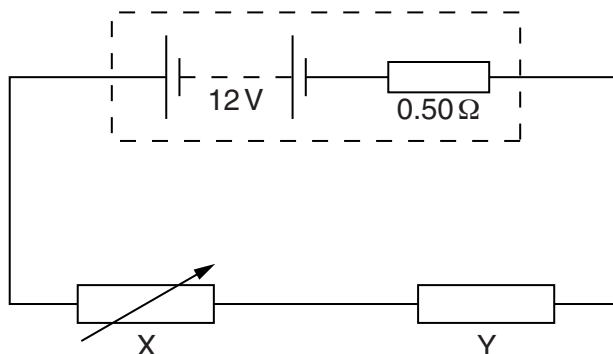


- 7 (a) A cell with internal resistance supplies a current. Explain why the terminal potential difference (p.d.) is less than the electromotive force (e.m.f.) of the cell.

.....  
.....  
..... [1]

- (b) A battery of e.m.f. 12 V and internal resistance  $0.50\ \Omega$  is connected to a variable resistor X and a resistor Y of constant resistance, as shown in Fig. 7.1.



**Fig. 7.1**

The resistance  $R$  of X is increased from  $2.0\ \Omega$  to  $16\ \Omega$ . The variation with  $R$  of the current  $I$  in the circuit is shown in Fig. 7.2.

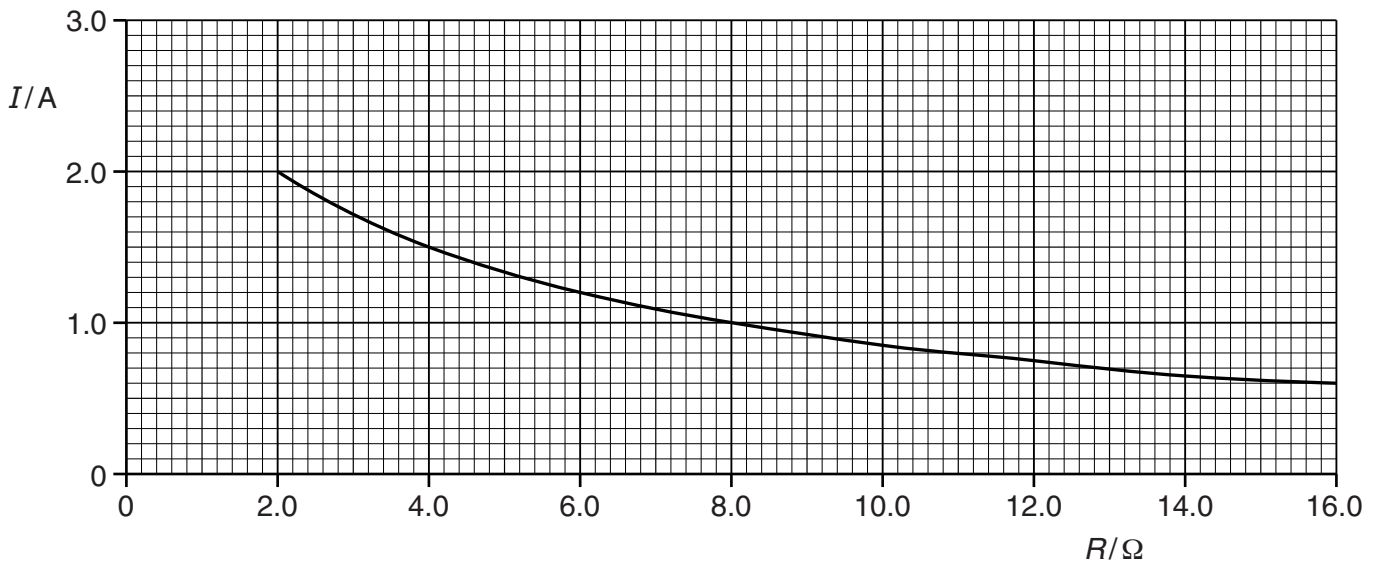


Fig. 7.2

Calculate, for  $I = 1.2\text{ A}$ ,

- (i) the p.d. across X,

p.d. = ..... V [2]

- (ii) the resistance of Y,

resistance = .....  $\Omega$  [3]

- (iii) the power dissipated in the battery.

power = ..... W [2]

- (c) Use Fig. 7.2 to explain the variation in the terminal p.d. of the battery as the resistance  $R$  of X is increased.

.....  
 ..... [1]