

**35** The resistance of a device is designed to change with temperature.

What is the device?

- A** a light-dependent resistor
- B** a potential divider
- C** a semiconductor diode
- D** a thermistor

**36** The diagram represents a circuit