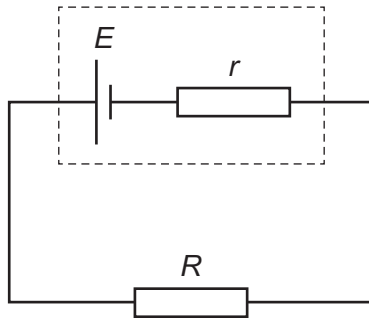


- 36** A cell of electromotive force (e.m.f.) E and internal resistance r is connected to a resistor of resistance R .

A maximum power P can be dissipated by the resistor without overheating.



What is the maximum value of E if the resistor does not overheat?

- A** $R\sqrt{\frac{P}{(R-r)}}$ **B** $R\sqrt{\frac{P}{(R+r)}}$ **C** $(R-r)\sqrt{\frac{P}{R}}$ **D** $(R+r)\sqrt{\frac{P}{R}}$