

5(a)	volt / ampere	B1
5(b)	$R = \rho L / A$	B1
	$(A = V / L)$	B1
	(so) $R = \rho L^2 / V$ (with ρ and V constant so $R \propto L^2$)	
5(c)(i)	$E = 2.4 \text{ V}$	A1
5(c)(ii)	$P = VI$ or I^2R or V^2 / R	C1
	$= 1.3 \times 5.0$ or $5.0^2 \times 0.26$ or $1.3^2 / 0.26$	C1
	$= 6.5 \text{ W}$	A1
5(c)(iii)	(–) internal resistance or (–) r	B1