

6(a)	potential difference applied between the plates	M1
	causes charge separation (between the plates) or causes energy to be stored (between the plates)	A1
6(b)(i)	$I = Q / t$	M1
	clear substitution of $Q = CV$ and $f = 1 / t$, leading to $I = fCV$	A1
6(b)(ii)	$2.5 \times 10^{-6} = 50 \times C \times 180$	C1
	$C = 280 \text{ pF}$	A1
6(c)	(total) capacitance increases	B1
	greater charge (for each cycle/discharge) so greater (average) current or V and f are constant so (average) current increases or I is (directly) proportional to C so (average) current increases	B1