

| Question | Answer                                                                | Marks       |
|----------|-----------------------------------------------------------------------|-------------|
| 5(a)     | <u>sum of</u> e.m.f.(s) = <u>sum of</u> p.d.(s)                       | <b>M1</b>   |
|          | around a loop / around a closed circuit                               | <b>A1</b>   |
| 5(b)(i)  | 1 $6.0 - 4.0I = 0$<br>$I = 1.5 \text{ A}$                             | <b>A1</b>   |
|          | 2 $6.0 + 6.0 = I (4.0 + R + 1.5)$<br>$12 = 1.5 (4.0 + R + 1.5)$       | <b>C1</b>   |
|          | $R = 2.5 \Omega$                                                      | <b>A1</b>   |
|          | or $6.0 = I (R + 1.5)$<br>$6.0 = 1.5 (R + 1.5)$                       | <b>(C1)</b> |
|          | $R = 2.5 \Omega$                                                      | <b>(A1)</b> |
|          | or    combines $6 = 4I$ and $6 = I(R + 1.5)$ to give<br>$4 = R + 1.5$ | <b>(C1)</b> |
|          | $R = 2.5 \Omega$                                                      | <b>(A1)</b> |

| Question  | Answer                                                                                | Marks     |
|-----------|---------------------------------------------------------------------------------------|-----------|
| 5(b)(ii)  | $I = Anvq$<br>ratio = $1^2 / 2^2$                                                     | <b>C1</b> |
|           | = 0.25                                                                                | <b>A1</b> |
| 5(b)(iii) | <u>total</u> (circuit) resistance increases                                           | <b>B1</b> |
|           | current / $I$ decreases or $P \propto I$ or $P \propto 1 / (\text{total resistance})$ | <b>M1</b> |
|           | power (transformed) decreases                                                         | <b>A1</b> |

| Question | Answer             | Marks     |
|----------|--------------------|-----------|
| 6(a)     | 1 / decreases by 1 | <b>A1</b> |