

Question	Answer	Marks
8(a)(i)	all frequencies have the same gain	B1
8(a)(ii)	output changes at the same time as input changes	B1
8(b)(i)	$R_T / 800 = 1.8 / 1.2$ $R_T = \mathbf{1200\ \Omega}$	A1
8(b)(ii)	stepped from -9 V to $+9\text{ V}$ or v.v.	B1
	V_{out} negative $< R_T$ and V_{out} positive $> R_T$	B1
8(b)(iii)	correct LED symbol with connection between V_{OUT} and earth	B1
	diode pointing upwards	B1

9702/42

Cambridge International AS/A Level – Mark Scheme

March 2018

PUBLISHED

Question	Answer	Marks
0(c)(i)	PCYV and QBYW	B1