

5(a)	volt / ampere	B1
5(b)	$R = \rho L / A$	C1
	$L = (1.8 \times 0.38 \times 10^{-6}) / 9.6 \times 10^{-7}$	C1
	= 0.71 m	A1
5(c)(i)	thermal energy is dissipated in resistor Y	B1
5(c)(ii)	$V / 1.2 = 1.8 / (1.8 + 0.6)$	C1
	$V = 0.90 \text{ V}$	A1
	or	
	$I = 1.2 / (1.8 + 0.6) (= 0.50)$	(C1)
	$V = 0.50 \times 1.8$ = 0.90 V	(A1)
5(d)(i)	remain the same	B1
5(d)(ii)	decrease	B1
5(e)(i)	$1 / R = 1 / 1.8 + 1 / 3.6$ $R = 1.2 \Omega$	A1

Question	Answer	Marks
5(e)(ii)	$I = 1.2 / (1.2 + 0.60)$	C1
	$= 0.67 \text{ A}$	A1
	or	
	$V_Y = 1.2 \times 0.60 / (1.2 + 0.60) (= 0.40)$	(C1)
	$I = 0.40 / 0.60$ $= 0.67 \text{ A}$	(A1)

Question	Answer	Marks
----------	--------	-------