

- 7 (a) (i) e.m.f. = energy / charge C1
 = $(1.6 \times 10^5) / (1.8 \times 10^4)$
 = 8.9 V A1
- (ii) current = $\Delta Q / \Delta t$ C1
 = $(1.80 \times 10^4) / (1.3 \times 10^5)$
 = 0.14 A A1 [4]
- (b) (i) energy $\propto R$ (or formula) C1
 energy = $(15 / 45) \times 1.14 \times 10^5$ C1
 = 3.7×10^4 J A1
- (ii) energy dissipated in internal resistance (of battery) B1 [4]
 OR in extra resistance in circuit