

5(a)	sum of e.m.f.(s) = sum of p.d.(s) or (algebraic) sum of e.m.f.(s) and p.d.(s) is zero	M1
	around a loop / around a <u>closed</u> circuit	A1
5(b)(i)	$1 / r_{(T)} = 1 / 0.59 + 1 / 0.59 + 1 / 0.59$	B1
	$(r_{(T)} =) 0.197 (\Omega)$ $(R =) 2.2 - 0.197 = 2.0 \Omega$	A1
	or	
	$I = 1.5 / 2.2 (= 0.68 \text{ A})$ and $i = 0.68 / 3$ (where I is the circuit current and i is the current from each cell)	(B1)
	$(E = IR + ir =) 1.5 = 0.68R + (0.68 / 3) \times 0.59$ and $R = 2.0 \Omega$	(A1)

PUBLISHED

Question	Answer	Marks
5(b)(ii)	current = $1.5 / 2.2$	C1
	= 0.68 A	A1
	or	
	p.d. across cell = p.d. across conductor $1.5 - 0.59I = 3I \times 2.0$ so $I = 0.228$ A (where I is current in cell) current = 3×0.228	(C1)
	= 0.68 A	(A1)
	or	
	current in conductor = $3 \times$ current in cell $V / 2.0 = 3 \times (1.5 - V) / 0.59$ (where V is p.d. across conductor) $V = 1.37$ V current = $1.37 / 2.0$	(C1)
	= 0.68 A	(A1)
5(c)(i)	$R = \rho L / A$	C1
	$R = 4\rho L / \pi d^2$ (ρ and L are the same so) $R_A / R_B = 7.6^2 / 4.3^2$	C1
	= 3.1	A1

PUBLISHED

Question	Answer	Marks
5(c)(ii)	$I = Anvq$ and I, n, q are same / equal / constant	B1
	$\frac{v_A}{v_B} = \frac{A_B}{A_A} = \frac{d_B^2}{d_A^2}$ ratio = $7.6^2 / 4.3^2$ = 3.1	A1
5(d)	combined internal resistance (of the cells) will be greater or total / circuit resistance (of circuit) greater (because a parallel resistance removed)	B1
	more 'lost volts' (inside each cell) or internal resistances take a greater share of total p.d. or conductor gets a smaller share of the total p.d. or current in <u>conductor</u> /total current decreases	M1
	(so) potential difference (across conductor) decreases	A1