

7(a)	$9.6 = 6.0 + (I \times 5800)$ or $3.6 = I \times 5800$	C1
	$I = 6.2 \times 10^{-4} \text{ A}$	A1
7(b)	$9.6 = 6.2 \times 10^{-4} \times (3400 + 5800 + R)$	C1
	or	
	$6.0 = 6.2 \times 10^{-4} \times (3400 + R)$	
	$R = 6.3 \times 10^3 \Omega$	A1
7(c)	$(\Delta E =) 9.6 \times 330 (= 3170 \text{ J})$	C1
	final stored energy = $2.6 \times 10^4 - 3170$ $= 2.3 \times 10^4 \text{ J}$	A1
7(d)(i)	decrease	B1
7(d)(ii)	decrease	B1
7(d)(iii)	increase	B1