

5(a)	$I_1 + I_2 = I_3$ [any subject]	B1
5(b)	$E_1 + E_3 = I_1R_1 + I_3R_3 + I_3R_4$ [any subject]	B1
5(c)	$E_1 - E_2 = I_1R_1 - I_2R_2$ [any subject]	B1