

11(a)(i)	circles drawn only around the top left and bottom right diodes	B1
11(a)(ii)	B shown as (+)ve and A shown as (–)ve	B1
11(b)(i)	$V_{\text{r.m.s.}} (= 5.6 / \sqrt{2}) = 4.0 \text{ V}$	A1
11(b)(ii)	$380 = 2\pi f$ or $f = 60.5 \text{ Hz}$	C1
	number $(= 2f) = 120$	A1
11(c)(i)	peak values (all) unchanged	B1
	(all) minima shown at 4.0 V	B1
	three lines from near peak showing concave curves after leaving dotted line not 'kinked' and not cutting the peak reaching <u>candidate's</u> minimum at the point where the decay meets the next dotted line	B1
	three lines drawn along the dotted lines showing rise in voltage from minima back to peak values	B1
11(c)(ii)	<u>mean</u> p.d. is higher or <u>r.m.s.</u> p.d. is higher or capacitor supplies energy <u>to resistor</u>	M1
	so (mean) power increases	A1