

7(a)	axes labelled with resistance and temperature	M0
	concave curve not touching temperature axis	A1
	line with negative gradient throughout	A1
7(b)	resistance of thermistor decreases	B1
	total circuit resistance decreases so voltmeter reading increases <i>or</i> current increases so voltmeter reading increases <i>or</i> greater proportion of resistance in fixed resistor so voltmeter reading increases <i>or</i> p.d. across thermistor decreases so voltmeter reading increases	B1
7(c)	(0.020 strain means) $\Delta R / R = 0.090$	C1
	$\Delta R = 0.090 \times 120 = 10.8 \, \Omega$	C1
	resistance = $120 + 10.8 = 130 \, \Omega$	A1