

10(a)	230 V	A1
10(b)	$\omega = 100\pi$ $T = \frac{2\pi}{\omega} = \frac{2\pi}{100\pi}$	C1
	= 0.020 s	A1
10(c)(i)	half-wave (rectification)	B1
10(c)(ii)	sinusoidal half waves in positive V only or negative V only, peak at 320 V	B1
	line at zero for second half of cycle	B1
	two time periods shown, each of 0.020 s	B1
10(c)(iii)	capacitor added in parallel with resistor	B1