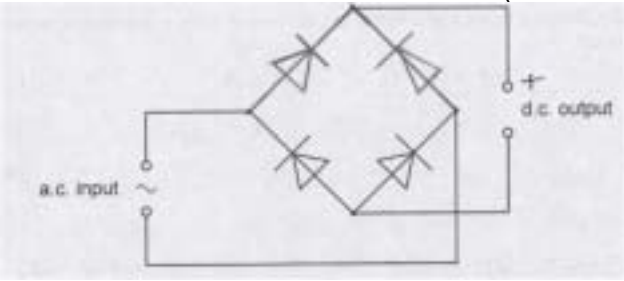


7(a)(i)	two diodes added in correct directions (Both diodes pointing inwards and upwards), correct symbols only 	B1
7(a)(ii)	'+' anywhere on upper output wire	B1
7(b)(i)	$\omega = 2\pi / T$ $= 2\pi / 2.5$ $= 0.80 \pi$ or $4\pi / 5$ or 2.5	C1
	(V =) 3.5 sin (0.8π t) or $3.5 \sin (4\pi t / 5)$ or $3.5 \sin (2.5 t)$	A1

PUBLISHED

Question	Answer	Marks
7(b)(ii)	$(P =) \frac{V^2}{2R}$ or $(P =) \frac{V_{r.m.s.}^2}{R}$	C1
	$= \frac{3.5^2}{2 \times 12}$ or $\frac{2.47^2}{12}$	
	= 0.51 W	A1

Question	Answer	Marks
----------	--------	-------