

7(a)	charge / potential	M1
	charge is on one plate, potential is p.d. between the plates	A1
7(b)(i)	$I = Q / t$	M1
	charge = CV <u>and</u> time = $1 / f$ leading to $I = fCV$	A1
7(b)(ii)	$4.8 \times 10^{-6} = 150 \times 60 \times C$	C1
	$C = 530 \text{ pF}$	A1
7(c)	(total) capacitance is halved	B1
	charge (for each cycle/discharge) is halved or since f and V are constant, current is proportional to capacitance	B1
	current = $2.4 \mu\text{A}$	B1