

7(a)(i)	full-wave (rectification)	B1
7(a)(ii)	lower left diode shown pointing left	B1
	lower right and upper left diodes shown pointing left	B1
7(a)(iii)	arrow indicating current direction in resistor to the right	B1
7(b)(i)	sketch: periodic line showing minimum $V_{OUT} = 0$ and maximum $V_{OUT} = +V_0$	B1
	line showing peak V_{OUT} at $t = 0, 0.5T, 1.0T, 1.5T$ and $2.0T$, with V_{OUT} going to zero half-way in between each peak	B1
	line showing correct modulated sine shape	B1
7(b)(ii)	sketch: sinusoidal curve with troughs sitting on the time axis	B1
	<u>peak</u> power at $t = 0, 0.5T, 1.0T, 1.5T$ and $2.0T$ and zero power half-way in between each peak	B1
7(b)(iii)	same power-time graph with or without rectification, so same V_{rms} or V^2 -time graph is same for both V_{OUT} and V_{IN} , so same V_{rms} or power does not depend on sign of V , so same V_{rms}	B1