

5(a)	sum of electromotive force(s) = sum of potential difference(s) around a (closed) loop.	B1
5(b)(i)	$R = V / I$	C1
	$= (9.0 - 4.0) / 1.1 \times 10^{-2}$	A1
	$= 450 \Omega$	
5(b)(ii)	resistance (of thermistor) = $25 (\Omega)$ (from graph)	C1
	$V = E \times R_Y / (R_Y + R_X)$ $= 9 \times 25 / (25 + 450)$ or $I = E / R_{\text{Total}} = 9 / (25 + 450) = 1.89 \times 10^{-2} \text{ A}$ $V = IR = 1.89 \times 10^{-2} \times 25$ or $V_{(X)} = 9 \times 450 / (25 + 450) = 8.53 \text{ V}$ $V = 9 - 8.53$	C1
	$V = 0.47 \text{ V}$	A1
5(b)(iii)	(resistance of X increases so) the <u>total</u> resistance increases	B1
	current decreases	B1
	potential difference (across thermistor / Y) decreases	B1