

7(a)	rectification (of the input voltage)	M1
	full-wave	A1
7(b)(i)	$P = V^2 / R$ or maximum $V = 9.0 \text{ V}$	C1
	$P_{\text{MAX}} = 9.0^2 / 370 = 0.22 \text{ W}$	A1
7(b)(ii)	sinusoidal shape with minima sitting on the time axis	B1
	correct frequency and phase, with minima at 0, 0.02, 0.04, 0.06 and 0.08 s and maxima at 0.01, 0.03, 0.05 and 0.07 s	B1
	all maxima shown at 0.22 W	B1
7(b)(iii)	mean power = peak power / 2 = $0.22 / 2$ = 0.11 W	A1
7(c)	power–time graph is identical	B1
	(so) mean powers are equal	B1