

6(a)(i)	charge per unit potential (difference)	M1
	charge on one plate <u>and</u> potential difference across the plates	A1
6(a)(ii)	any three points from: • smoothing • timing/(time) delay • tuning • oscillator • blocking d.c. • surge protection • temporary power supply	B3
6(b)	(capacitors in series have combined capacitance =) $8\ \mu\text{F}$	C1
	capacitance = $8 + 24$ $= 32\ \mu\text{F}$	A1

Question	Answer	Marks
----------	--------	-------