

7(a)	two resistors connected in series between earth and positive of battery and no extra connections	B1
	one resistor and thermistor connected in series between earth and positive of battery and no extra connections	B1
	midpoints of the two potential dividers connected, one each, to the op-amp input terminals	B1
	thermistor in correct place in potential divider circuit (either the upper part of the potential divider leading to V^+ or the lower part of the potential divider leading to V^-)	B1
7(b)(i)	value greater than $1000\ \Omega$	A1
7(b)(ii)	non-zero value less than $1000\ \Omega$	A1