

6(a)(i)	charge per unit potential (difference)	M1
	charge on one plate and potential difference between the plates	A1
6(a)(ii)	any three points from: • smoothing • timing/(time) delaying • tuning • oscillator • blocking d.c. • surge protection • temporary power supply	B3
6(b)(i)	parallel combination of two in series and a single capacitor	B1
6(b)(ii)	one capacitor in series with two in parallel	B1

Question	Answer	Marks
-----------------	---------------	--------------