

5(a)(i)	$Q = CV$	C1
	$Q_0 = 24 \times 470 \times 10^{-6}$ $= 0.011 \text{ C}$	A1
5(a)(ii)	$I_0 = 24 / 5600$ $= 4.3 \times 10^{-3} \text{ A}$	A1
5(a)(iii)	$\tau = RC$	C1
	$= 5600 \times 470 \times 10^{-6}$ $= 2.6 \text{ s}$	A1
5(a)(iv)	line with negative gradient throughout passing through $(0, I_0)$	B1
	exponential decay curve asymptotic to t -axis	B1
5(b)(i)	current in wire P gives rise to a magnetic field	B1
	as current (in P) changes, wire Q cuts (magnetic) flux (of wire P)	B1
	cutting magnetic flux causes induced e.m.f. (across Q)	B1
5(b)(ii)	sketch shows line with a negative gradient throughout	B1