

Question	Answer	Marks
6(a)	potential difference per unit current	B1
6(b)(i)	$\rho = RA / L$	C1
	$= (0.33 \times 8.0 \times 10^{-6}) / 2.4$ $= 1.1 \times 10^{-6} \Omega \text{ m}$	A1
6(b)(ii)	$Q = It$	C1
	$= 4.7 \times 5.0 \times 60$ $= 1400 \text{ C}$	A1
6(b)(iii)	$I = nAvq$ $n = 4.7 / (8.0 \times 10^{-6} \times 0.16 \times 10^{-3} \times 1.60 \times 10^{-19})$	C1
	$= 2.3 \times 10^{28} \text{ m}^{-3}$	A1
6(c)(i)	correct symbols for resistor and thermistor, shown correctly connected in series with the battery	B1
6(c)(ii)	(as temperature increases) resistance of thermistor decreases	M1
	(total resistance decreases so) greater current (in circuit/wire) so power (dissipated in the wire) increases or (total resistance decreases so) greater (share of) p.d. across wire so power (dissipated in the wire) increases	A1

9702/23

Cambridge International AS & A Level – Mark Scheme

October/November 2024

PUBLISHED

Question	Answer	Marks