

7(a)	• infinite (open-loop) gain • infinite slew rate • infinite input impedance • zero output impedance • infinite bandwidth <i>Any two points, 1 mark each</i>	B2
7(b)	X: thermistor and Y: relay	B1
7(c)(i)	(any) difference in voltage at the inputs causes output to saturate (because gain is very large)	B1
	saturates positively if $V^+ > V^-$ <u>and</u> saturates negatively if $V^+ < V^-$	B1
7(c)(ii)	comparator	B1
7(c)(iii)	temperature	M1
	above a particular value	A1
7(c)(iv)	to adjust the temperature (at which the lamp illuminates/extinguishes)	B1