

6	(a) p.d. = work (done) / charge OR energy transferred from (electrical to other forms) / (unit) charge	B1	[1]
	(b) (i) $R = \rho l / A$ $\rho = 18 \times 10^{-9}$ $R = (18 \times 10^{-9} \times 75) / 2.5 \times 10^{-6} = 0.54 \, \Omega$	C1	
		C1	
		A1	[3]
	(ii) $V = IR$ $R = 38 + (2 \times 0.54)$ $I = 240 / 39.08 = 6.1 \, (6.14) \, A$	C1	
		C1	
		A1	[3]

Page 4	Mark Scheme	Syllabus	Paper
	GCE AS/A LEVEL – October/November 2013	9702	21

(iii) $P = I^2 R$ or $P = VI$ and $V = IR$ or $P = V^2/R$ and $V = IR$ C1
 $= (6.14)^2 \times 2 \times 0.54$ C1
 $= 41 \text{ (40.7) W}$ A1 [3]

(c) area of wire is less (1/5) hence resistance greater ($\times 5$) M1
OR R is $\propto 1/A$ therefore R is greater
p.d. across wires greater so power loss in cables increases A1 [2]