

9	(a) operates on / takes signal from sensing device (so that) it gives an voltage output	B1 B1	[2]
	(b) thermistor and resistor in series between +4 V line and earth V_{OUT} shown clearly across <i>either</i> thermistor <i>or</i> resistor V_{OUT} shown clearly across thermistor	M1 A1 A1	[3]
	(c) e.g. remote switching switching large current by means of a small current isolating circuit from high voltage switching high voltage by means of a small voltage/current (<i>any two sensible suggestions, 1 each to max. 2</i>)	B2	[2]