

6 (a)	sketch: peaks in opposite directions in correct regions	B1	
	no e.m.f. when current constant	B1	
	correct shape for <u>one</u> of the pulses	B1	[3]
(b)	(i) <u>two</u> correct diodes circled	B1	[1]
	(ii) $V_{\max} = \sqrt{2} \times V_{\text{rms}}$	C1	
	$= 8.48 \text{ V}$	A1	[2]
	(iii) capacitor connected across SQ	B1	
	discharges through load when p.d. / current in load reduces	B1	
	thus maintains p.d. across load (or other relevant comment)	B1	[3]