

- 6 (a) power = VI C1
current = $10.5 \times 10^3 / 230$ M1
= 45.7 A A0 [2]
- (b) (i) p.d. across cable = 5.0 V C1
 $R = 5.0 / 46$ C1
= 0.11 Ω A1 [3]
- (ii) $R = \rho L / A$ C1
 $0.11 = (1.8 \times 10^{-8} \times 16 \times 2) / A$ C1
 $A = 5.3 \times 10^{-6} \text{ m}^2$ A1 [3]
(wires in parallel, not series, allow max 1/3 marks)

Page 4	Mark Scheme	Syllabus	Paper
	GCE A/AS LEVEL – October/November 2007	9702	02

(c) (i) *either* $\text{power} = V^2 / R$ *or* $\text{power} \propto V^2$ C1
ratio = $(210 / 230)^2 = 0.83$ A1 [2]

(ii) resistance of cable is greater M1
greater power loss/fire hazard/insulation may melt
wire may melt/cable gets hot A1 [2]

7 (a) most α -particles deviated through small angles B1