

8(a)(i)	gain is the same for all frequencies	B1
8(a)(ii)	no (time) delay in change in output when input is changed	B1
8(b)(i)	(at saturation,) $V_{OUT} = 5.0 \text{ V}$	C1
	gain = $5.0 / 0.40$ = 12.5 or 13	A1
8(b)(ii)	$12.5 = 1 + (R / 800)$	C1
	$R = 9200 \Omega$	A1

Question	Answer	Marks
----------	--------	-------