

7(a)	output signal proportional to input signal	B1
	output signal has same sign/polarity as input signal	B1
7(b)(i)	$\text{gain} = V_{\text{OUT}} / V_{\text{IN}}$ $= 2.6 / 0.084$ $= 31$	A1
7(b)(ii)	$31 = 1 + (15 \times 10^3) / R$	C1
	$R = 500 \Omega$	A1
7(c)(i)	e.g. cathode-ray oscilloscope/CRO	B1
7(c)(ii)	gain is reduced	B1
	(so) V_{OUT} is smaller	B1