

8(a)(i)	constant gain for all frequencies	B1
8(a)(ii)	unchanged	B1
8(b)(i)	(open loop) gain of op-amp is infinite	B1
	feedback loop ensures $V^+ \approx V^-$ or any difference between V^+ and V^- results in saturated output	B1
	non-inverting input is 0 V so inverting input also at 0 V	B1
8(b)(ii)	input = $(40 \times 1.5) / (40 + 110)$	C1
	= 0.40 V	A1
8(b)(iii)	gain = $(-)(100 + 230) / 150$ or feedback current = $0.40 / (150 \times 10^3)$ (A)	C1
	p.d. = $[(100 + 230) / 150] \times 0.40$ = 0.88 V	A1
8(c)	(magnitude of) gain decreases	M1
	voltmeter reading decreases	A1