

6(a)	<u>sum of</u> current(s) entering a junction = <u>sum of</u> current(s) leaving (the same junction) or (algebraic) sum of current (s) at a junction is zero	B1
6(b)	(by Kirchhoff's second law) $V = V_1 + V_2$	B1
	so $IR_T = IR_1 + IR_2$ (and cancelling I gives) $R_T = R_1 + R_2$ or $V/I = V_1/I + V_2/I$ (and substituting R gives) $R_T = R_1 + R_2$	B1
6(c)	current in circuit = $1.35 / (10 + 15)$ (= 0.054 A)	C1
	$r = (E - V) / I$	C1
	$= (1.5 - 1.35) / 0.054$ $= 2.8 \Omega$	A1
	or	
	by potential divider principle $\frac{0.15}{1.35} = \frac{r}{25}$	(C2)
	$r = 2.8 \Omega$	(A1)
	or	
	$I = 1.35 / (10 + 15)$ (= 0.054 A)	(C1)
	total resistance = $1.50 / 0.054$ (= 27.8 Ω) $r = 27.8 - 25$	(C1)
	$r = 2.8 \Omega$	(A1)

PUBLISHED

Question	Answer	Marks
6(d)(i)	the (total) resistance (of the circuit) has decreased (and e.m.f. is unchanged)	M1
	(the current (in the cell) will) increase	A1
6(d)(ii)	(as the current is greater and so there is a) larger p.d. across the internal resistance	M1
	(terminal p.d. will) decrease	A1