

5	(a)	the (value of the) direct current that dissipates (heat) energy at the same rate (in a resistor) <i>allow 'same power' and 'same heating effect'</i>	M1 A1	[2]
	(b)	$\sqrt{2}I_{\text{rms}} = I_0$	B1	[1]
	(c)	(i) power $\propto I^2$ or $P = I^2 R$ or $P = VI$ ratio = 2.0 (allow 1 s.f.)	C1 A1	[2]
		(ii) advantage: e.g. easy to change the voltage disadvantage: e.g. cables require greater insulation rectification – with some justification	B1	[2]
	(d)	(i) 3.0 A (allow 1 s.f.) (ii) 3.0 A (allow 1 s.f.)	A1 A1	[2]
Total				[9]
6		0 - + (-1 for each error) + - 0 (-1 for each error)	B2 B2	